

# Transfer Functions

## Agenda

- Transfer Functions
- A Couple of Examples
- Circuit Analysis Using MATLAB LTI Transfer Function Block
- Circuit Simulation Using Simulink Transfer Function Block

## Transfer Functions for Circuits

When doing circuit analysis with components defined in the complex frequency domain, the ratio of the output voltage  $V_{\text{out}}(s)$  to the input voltage  $V_{\text{in}}(s)$  *under zero initial conditions* is of great interest. This ratio is known as the *voltage transfer function* denoted  $G_v(s)$ :

$$G_v(s) = \frac{V_{\text{out}}(s)}{V_{\text{in}}(s)}$$

Similarly, the ratio of the output current  $I_{\text{out}}(s)$  to the input current  $I_{\text{in}}(s)$  *under zero initial conditions*, is called the *current transfer function* denoted  $G_i(s)$ :


$$G_i(s) = \frac{I_{\text{out}}(s)}{I_{\text{in}}(s)}$$

In practice, the current transfer function is rarely used, so we will use the voltage transfer function denoted:

$$G(s) = \frac{V_{\text{out}}(s)}{V_{\text{in}}(s)}$$
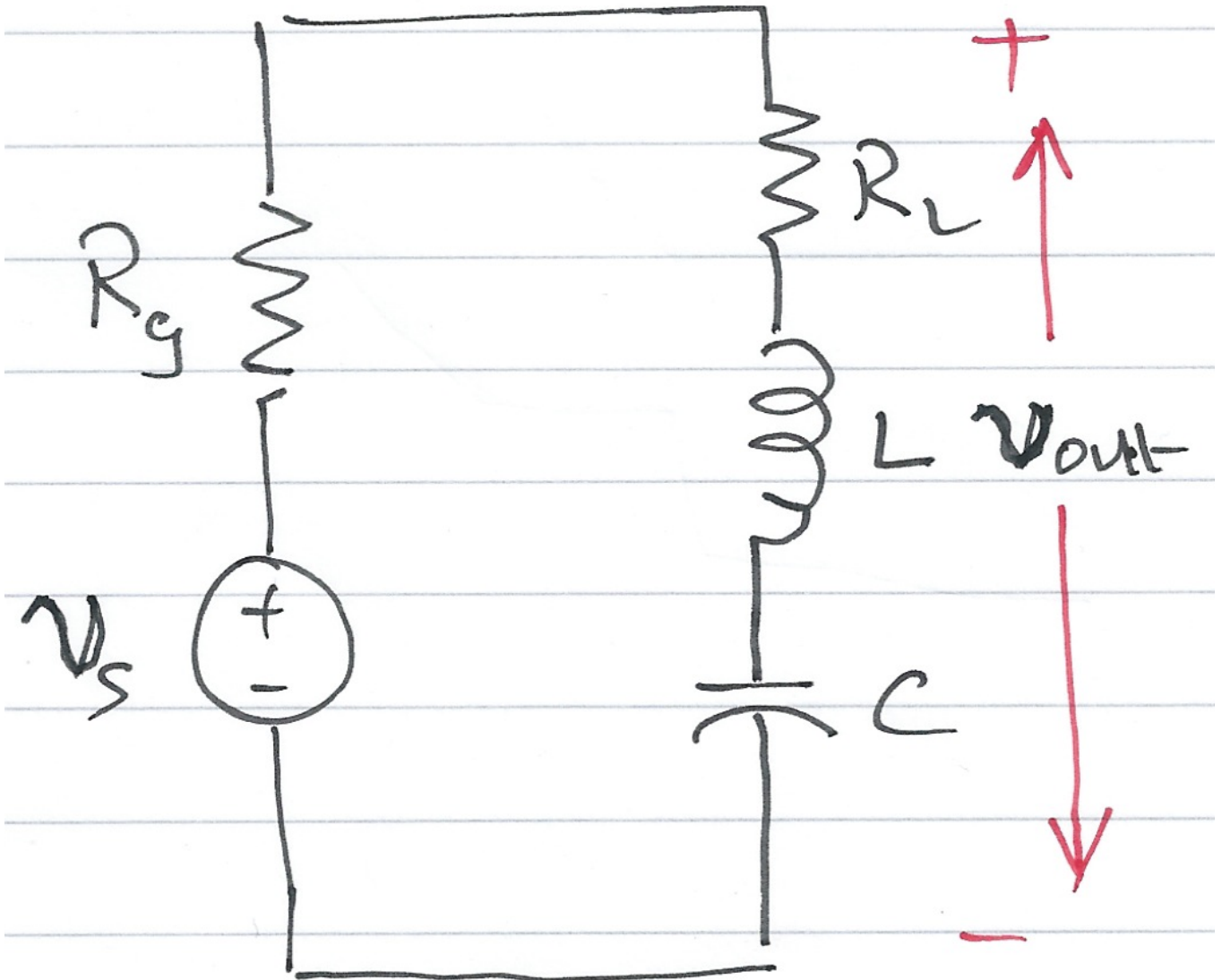
### Example 6

Derive an expression for the transfer function  $G(s)$  for the circuit below. In this circuit  $R_g$  represents the internal resistance of the applied (voltage) source  $v_s$ , and  $R_L$  represents the resistance of the load that consists of  $R_L$ ,  $L$  and  $C$ .






### Sketch of Solution

- Replace  $v_s(t)$ ,  $R_g$ ,  $R_L$ ,  $L$  and  $C$  by their transformed (*complex frequency*) equivalents:  $V_s(s)$ ,  $R_g$ ,  $R_L$ ,  $sL$  and  $1/(sC)$
- Use the *Voltage Divider Rule* to determine  $V_{\text{out}}(s)$  as a function of  $V_s(s)$
- Form  $G(s)$  by writing down the ratio  $V_{\text{out}}(s)/V_s(s)$

### Example 7

Compute the transfer function for the op-amp circuit shown below in terms of the circuit constants  $R_1$ ,  $R_2$ ,  $R_3$ ,  $C_1$  and  $C_2$ . Then replace the complex variable  $s$  with  $j\omega$ , and the circuit constants with their numerical values and plot the magnitude  $|G(s)| = |V_{out}(s)/V_{in}(s)|$  versus radian frequency  $\omega$ .

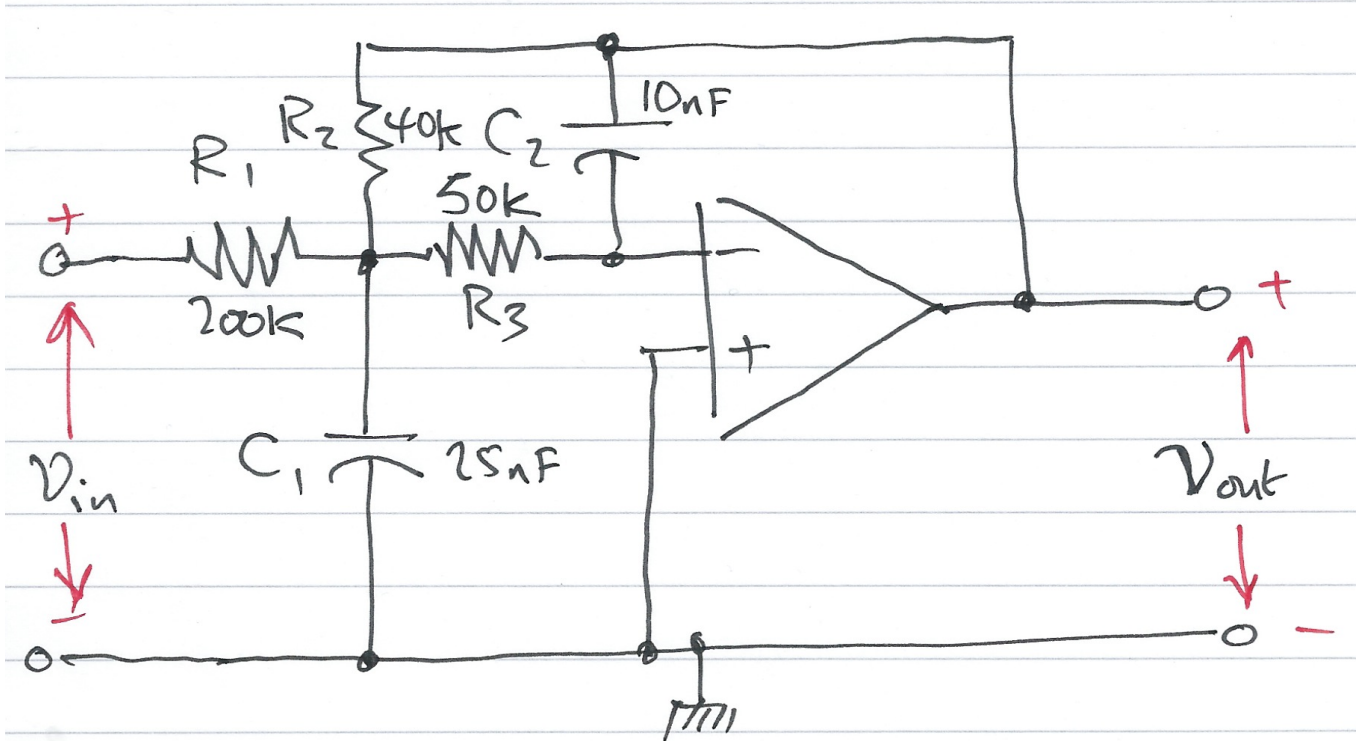




## Sketch of Solution

- Replace the components and voltages in the circuit diagram with their complex frequency equivalents
- Use nodal analysis to determine the voltages at the nodes either side of the 50K resistor  $R_3$
- Note that the voltage at the input to the op-amp is a virtual ground
- Solve for  $V_{\text{out}}(s)$  as a function of  $V_{\text{in}}(s)$
- Form the reciprocal  $G(s) = V_{\text{out}}(s)/V_{\text{in}}(s)$
- Use MATLAB to calculate the component values, then replace  $s$  by  $j\omega$ .
- Plot  $|G(j\omega)|$  on log-linear "paper"
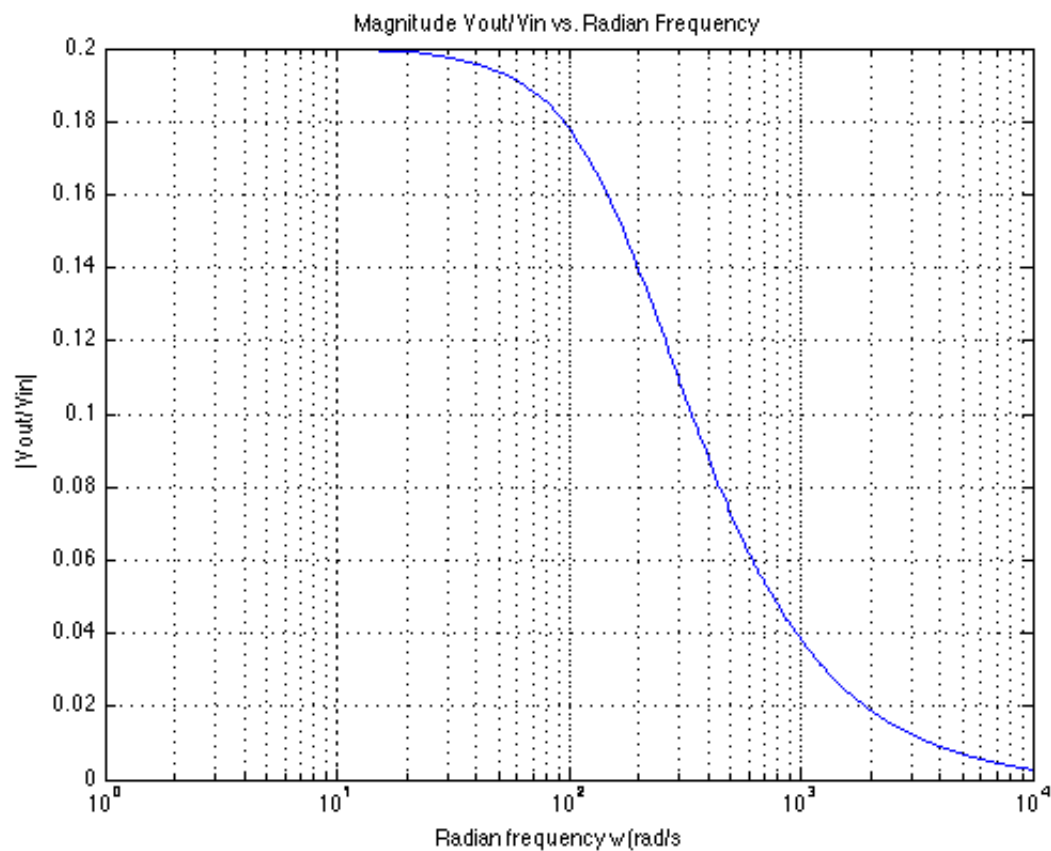
## The Matlab Bit

See attached script: [solution7.m](#) (matlab/solution7.m).



## Using Transfer Functions in Matlab for System Analysis

Please use the file [tf\\_matlab.m](#) (matlab/tf\_matlab.m) to explore the Transfer Function features provide by Matlab. Use the *publish* option to generate a nicely formatted document.

# Using Transfer Functions in Simulink for System Simulation



The Simulink transfer function (**Transfer Fcn**) block shown above implements a transfer function representing a general input output function

$$G(s) = \frac{N(s)}{D(s)}$$

that it is not specific nor restricted to circuit analysis. It can, however be used in modelling and simulation studies.

## Example

Recast Example 7 as a Matlab problem using the LTI Transfer Function block. For simplicity use parameters  $R_1 = R_2 = R_3 = 1 \, \Omega$  and  $C_1 = C_2 = 1 \, \text{F}$ . Calculate the step response using the LTI functions.

The Matlab solution: [example8.m \(matlab/example8.m\)](#)

Verify the result with Simulink.